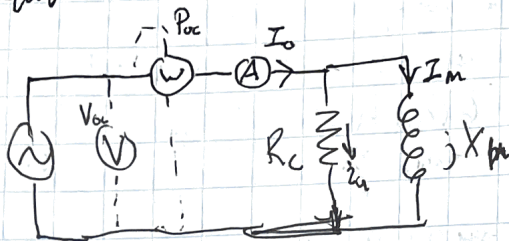


Prelab 2 Xformer Approximation

Req'd Circuit Parameters




$$R_c = \frac{V_{in}^2}{P_{loss}}$$

$$I_a = \frac{V_{in}}{R_c} \quad I_m = \sqrt{I_o^2 - I_a^2}$$


$$X_m = \frac{V_{in}}{I_m} = \frac{V_{in}}{\sqrt{I_o^2 - I_a^2}} = \frac{V_{in}}{\sqrt{I_o^2 - \left(\frac{V_{in}^2}{P_{loss}}\right)^2}}$$

$$X_m = \frac{V_{in}}{\sqrt{I_o^2 - \left(\frac{P_{loss}}{V_{in}}\right)^2}}$$

OC Test

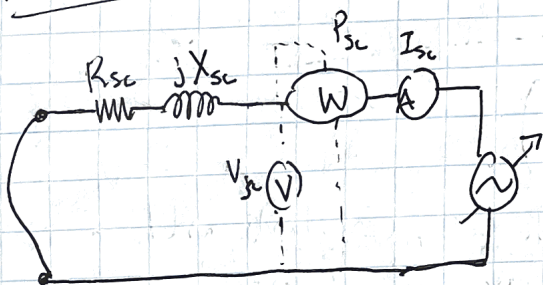

$$R_{sc} = \frac{P_{sc}}{I_{sc}^2}$$

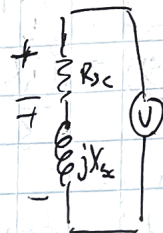

$$X_{sc} = \sqrt{Z_{sc}^2 - R_{sc}^2}$$

$$V_{sc} = Z_{sc} I_{sc}$$

$$Z_{sc} = R_{sc} + jX_{sc}$$

$$V_{sc} = \sqrt{V_a^2 + V_m^2}$$

$$V_{sc} = R_{sc} I_{sc} + jX_{sc} I_{sc}$$

$$I_m X_{sc} = V_{sc}$$

$$\frac{V_m}{I_{sc}} = \sqrt{\frac{V_{sc}^2 - V_a^2}{I_{sc}^2}} = X_{sc}$$

$$X_{sc} = \frac{V_{sc}}{I_{sc}} = \frac{V_{sc}}{\sqrt{I_{sc}^2 - \left(\frac{P_{sc}}{V_{sc}}\right)^2}}$$

$$X_{sc} = \frac{V_{sc}}{\sqrt{I_{sc}^2 - \left(\frac{P_{sc}}{V_{sc}}\right)^2}}$$


$$V_a = R_{sc} I_{sc} = \frac{P_{sc}}{I_{sc}}$$

$$\alpha = \frac{V_{oc, HV}}{V_{oc, LV}}$$

Lab 2 Prelab Pt 2

Current in an ideal inductor being supplied by a sinusoidal voltage
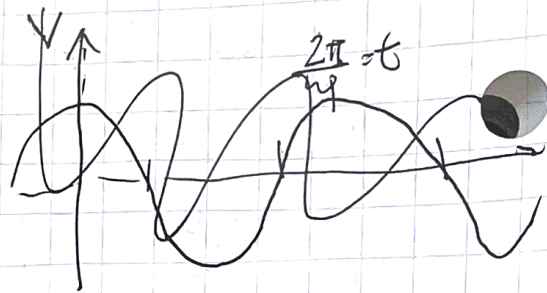
$$V = L \frac{di}{dt} \quad \text{if } V = V_0 \sin(\omega t)$$



a) The inductor is energized when the Applied Voltage is at its peak

$$\text{Peak} = t = 0, \frac{2\pi}{\omega}, \dots$$

$$i = \frac{1}{L} \int V dt = \frac{1}{L} \int V_0 \sin(\omega t) dt$$

→ When an inductor is "Fully charged" = energized

$$V = N \frac{d\Phi}{dt} \quad \Phi = \frac{1}{N} \int V(t) dt = \left(\frac{V_0}{N\omega} [\cos(\pi) - \cos(t_0)] \right)$$


$t_0 = \omega t_0$
By Substitution

b) Inductor fully energized when the Voltage Reaches zero


$$\text{if } t_0 = 0 \quad \text{at } \pi \quad \Phi = 2\Phi_m$$

$$\text{else if } t_0 = \frac{\pi}{2} \quad \Phi = \Phi_m$$

$$\Phi_m = \frac{V_0}{N\omega}$$

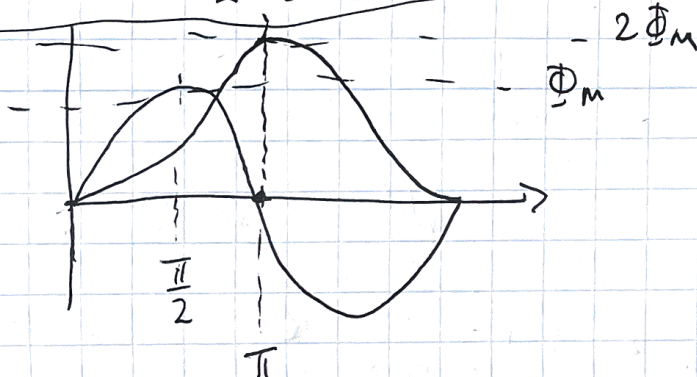

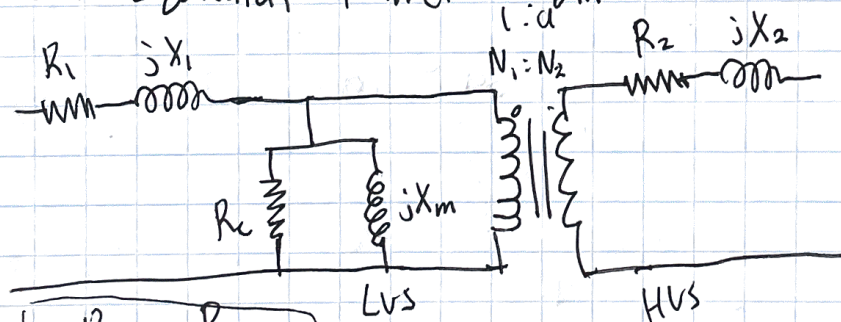Circuit Equivalent Parameters $\frac{V_1}{N_1} = \frac{V_2}{N_2}$ HVS = more turns side



$$R_1 = \frac{R_{sc}}{2a^2}$$

$$R_2 = \frac{R_{sc}}{2}$$

$$X_1 = \frac{X_{sc}}{2a^2}$$

$$X_2 = \frac{X_{sc}}{2}$$

R_c = Calculated value

X_m = Calculated value